

ECE 3050 Analog Electronics Quiz 2


September 2, 2009

Professor Leach Last Name: _____ First Name: _____

Instructions. Print your name in the spaces above. Place a box around any answer. **Honor Code Statement:**

I have neither given nor received help on this quiz. Initials _____

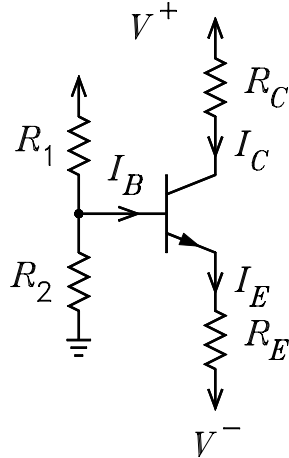- 1 of 2. Given $V^+ = 22\text{ V}$, $V^- = -15\text{ V}$, $R_1 = 220\text{ k}\Omega$, $R_2 = 22\text{ k}\Omega$, $R_C = 12\text{ k}\Omega$, $\alpha = 0.99$, $\beta = 99$, and $V_{BE} = 0.65\text{ V}$.
- (a) Solve for R_E for $I_C = 1.3\text{ mA}$.
- (b) Verify that the BJT is biased in its active mode.



$$\begin{aligned}
 V_p &:= 22 & V_n &:= -15 & R_1 &:= 220000 & R_2 &:= 22000 & R_C &:= 12000 \\
 \alpha &:= 0.99 & \beta &:= 99 & V_{BE} &:= 0.65 & I_C &:= 0.0013 \\
 V_{BB} &:= V_p \cdot \frac{R_2}{R_1 + R_2} & R_{BB} &:= R_{p2}(R_1, R_2) & V_{BB} &= 2 & R_{BB} &= 2 \cdot 10^4 \\
 V_{BB} - V_n &= \frac{I_C}{\beta} \cdot R_{BB} + V_{BE} + \frac{I_E}{\alpha} \cdot R_E \\
 R_E &:= \frac{V_{BB} - V_n - \frac{I_C}{\beta} \cdot R_{BB} - V_{BE}}{\frac{I_C}{\alpha}} & R_E &= 1.225 \cdot 10^4 \\
 V_{CB} &:= (V_p - I_C \cdot R_C) - \left(V_n + \frac{I_C}{\alpha} \cdot R_E \right) & V_{CB} &= 5.313
 \end{aligned}$$

- 2 of 2. (a) The MOSFET drain current is given by $i_D = K (v_{GS} - V_{TO})^2$. If you are given i_D , there are two solutions to the equation for v_{GS} . What determines the correct one? [The solution for which $v_{GS} > V_{TO}$.]
- (b) The gate-source loop bias equation for the MOSFET is $V_{GG} - V_{SS} = V_{GS} + I_D R_{SS}$. When it is used with the equation in part (a), show that this equation leads to a quadratic equation that must be solved for I_D . You do not have to solve the quadratic equation.

$$I_D R_{SS} + \frac{1}{\sqrt{K}} \sqrt{I_D} - (V_{GG} - V_{SS} - V_{TO}) = 0$$