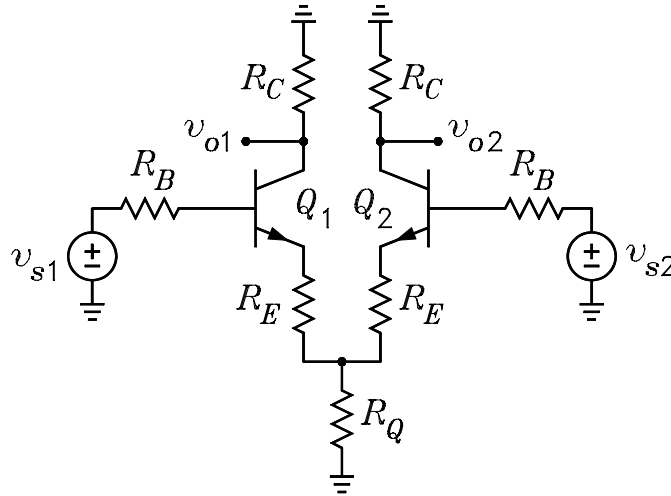


ECE3050 Homework Set 9

1. The figure shows the ac signal circuit of a BJT differential amplifier. It is given that $V_T = 0.025\text{ V}$, $\beta = 99$, $r_x = 30\ \Omega$, $I_E = 1.5\text{ mA}$, $R_B = 1.5\text{ k}\Omega$, $R_E = 50\ \Omega$, $R_C = 12\text{ k}\Omega$, and $R_Q = 10\text{ k}\Omega$. To simplify the problem, assume that that $r_0 = \infty$.

- (a) Show that $r'_e = 31.967\ \Omega$.
- (b) Show that the Thévenin equivalent circuits seen looking out of the emitters in the ac signal circuit consist of the voltages and resistances $v_{te1} = 0.992v_{s2}$, $v_{te2} = 0.992v_{s1}$, and $R_{te1} = R_{te2} = 131.3\ \Omega$.
- (c) Use the emitter equivalent circuits on the simplified T model to show that $i'_{e1} = (v_{s1} - 0.992v_{s2})/163.267$ and $i'_{e2} = (v_{s2} - 0.992v_{s1})/163.267$.
- (d) Use the collector equivalent circuits of the simplified T model to show that $v_{o1} = -72.764v_{s1} + 72.173v_{s2}$ and $v_{o2} = -72.764v_{s2} + 72.173v_{s1}$.



2. An alternate solution to the differential amplifier of Problem 1 is to use common-mode and differential.

- (a) For the common-mode input signals $v_{s1} = v_{s2} = v_{s(cm)}$, use the simplified T model to show that the common-mode gain to each output is given by

$$A_{cm} = \frac{v_{o1}}{v_{s(cm)}} = \frac{v_{o2}}{v_{s(cm)}} = -0.592$$

- (b) For the differential input signals $v_{s1} = v_{s(d)}/2$ and $v_{s2} = -v_{s(d)}/2$, use the simplified T model to show that the differential gain is given by

$$A_d = \frac{v_{o1}}{v_{s(d)}} = -\frac{v_{o2}}{v_{s(d)}} = -72.468$$

- (c) Solve for the common-mode rejection ratio at the v_{o1} output to show that

$$CMRR = \frac{|v_{o1}/v_{s(d)}|}{|v_{o1}/v_{s(cm)}|} = \frac{|v_{o2}/v_{s(d)}|}{|v_{o2}/v_{s(cm)}|} = 122.501 = 41.763\text{ dB}$$

(d) For $v_{s(cm)} = (v_{s1} + v_{s2})/2$ and $v_{s(d)} = v_{s1} - v_{s2}$, show that

$$\begin{aligned} v_{o1} &= \left(A_d + \frac{A_{cm}}{2}\right)v_{s1} - \left(A_d - \frac{A_{cm}}{2}\right)v_{s2} = -72.764v_{s1} + 72.173v_{s2} \\ v_{o2} &= -\left(A_d - \frac{A_{cm}}{2}\right)v_{s1} + \left(A_d + \frac{A_{cm}}{2}\right)v_{s2} = 72.173v_{s1} - 72.764v_{s2} \end{aligned}$$

(e) Show that

$$v_{o(d)} = v_{o1} - v_{o2} = -144.937(v_{s1} - v_{s2})$$

3. A differential amplifier has a differential gain of -100 and a common-mode gain of -0.01 . The input voltages are given by $v_{i1} = 0.1 \sin \omega_1 t - 0.01 \sin \omega_2 t$ and $v_{i2} = 0.1 \sin \omega_1 t + 0.01 \sin \omega_2 t$.

(a) Show that the differential and common-mode input voltages are given by

$$v_{id} = -0.02 \sin \omega_2 t \quad v_{icm} = 0.1 \sin \omega_1 t$$

(b) If the output is taken from the collector of Q_1 , show that


$$v_{o1} = -0.001 \sin \omega_1 t + 2 \sin \omega_2 t$$

(c) If the ω_1 term is an unwanted interference signal and the ω_2 term is a desired signal, show that the input signal-to-noise ratio is $SNR_{in} = -14$ dB, which is pretty low. Show that the output signal-to-noise ratio is $SNR_{out} = 66$ dB.

(d) Show that the improvement in the signal-to-noise ratio between the input and the output is 80 dB. Note: This problem illustrates how a common-mode noise voltage on a signal pair can be reduced by a large amount with a differential amplifier input stage.

(e) What is the $CMRR$? Answer: 80 dB.

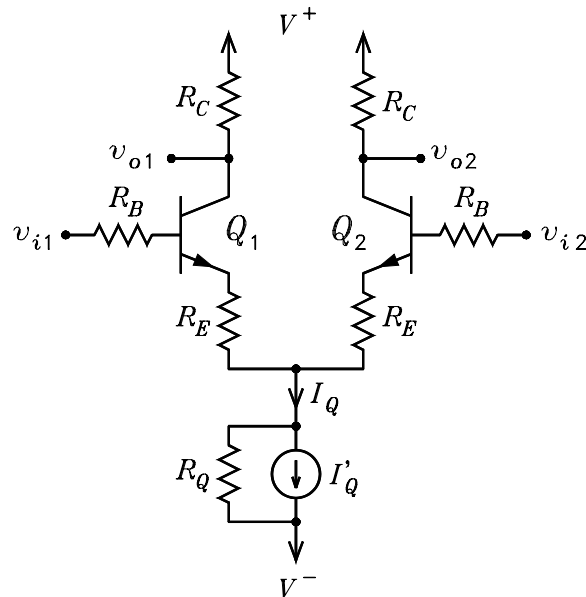4. For the diff amp shown, it is given that $I'_Q = 1.8$ mA, $R_Q = 20$ k Ω , $R_C = 7500$ Ω , $R_E = 30$ Ω , $R_B = 100$ Ω , $r_x = 20$ Ω , $V^+ = +15$ V, $V^- = -15$ V, $V_{BE} = 0.65$ V, $\beta = 149$, $V_A = \infty$, and $V_T = 25$ mV.



- (a) With $v_{i1} = v_{i2} = 0$, show that $I_{E1} = I_{E2} = 1.258 \text{ mA}$, $r_0 = \infty$, $r_e = 19.876 \Omega$, $r'_e = 21.076 \Omega$, and $r_{ib} = 15.08 \text{ k}\Omega$.
- (b) Show that $R_{te} = 80.946 \Omega$ for each BJT, $v_{te1} = 0.997v_{i2}$, and $v_{te2} = 0.997v_{i1}$.
- (c) Show that $i'_c/v_{tb} = -i'_c/v_{te} = 9.704 \times 10^{-3} \Omega$ for each BJT.
- (d) Show that $v_{o1}/v_{i1} = v_{o2}/v_{i2} = -72.778$ and $v_{o2}/v_{i1} = v_{o1}/v_{i2} = +72.593$.
- (e) If the output is taken from either the collector of Q_1 or the collector of Q_2 , show that $CMRR = 392.071$ or 51.876 dB .
- (f) For $v_{i1} = v_{i(d)}/2$ and $v_{i2} = -v_{i(d)}/2$, show that the differential input resistance between the two inputs in series is $r_{i(d)} = 10.2 \text{ k}\Omega$.
- (g) For $v_{i1} = v_{i2} = v_{i(cm)}$, show that the common-mode input resistance to the two inputs in parallel is $r_{i(cm)} = 4.005 \text{ M}\Omega$.