

Common-Collector Amplifier Example - Summer 2000

$$R_p(x,y) := \frac{x \cdot y}{x + y}$$


Function for calculating parallel resistors.

$$R_1 := 100000 \quad R_2 := 120000 \quad R_C := 0 \quad R_E := 5600 \quad R_S := 5000 \quad R_L := 10000$$

$$V_p := 15 \quad V_m := -15 \quad V_{BE} := 0.65 \quad V_T := 0.025 \quad \beta := 99 \quad \alpha := 0.99$$

$$r_x := 20 \quad r_o := 50000$$
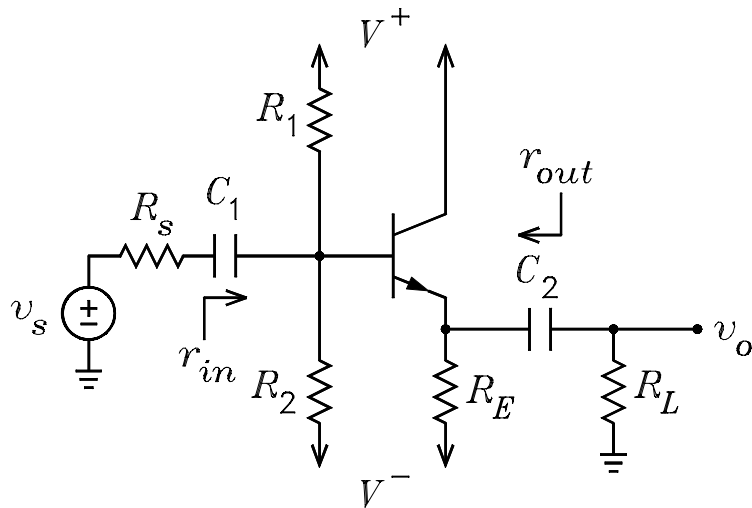
$$v_s := 1 \quad \text{With } v_s = 0, \text{ the voltage gain is equal to } v_o.$$



DC Bias Solution

$$V_{BB} := \frac{V_p \cdot R_2 + V_m \cdot R_1}{R_1 + R_2} \quad V_{BB} = 1.364$$

$$R_{BB} := R_p(R_1, R_2) \quad R_{BB} = 5.455 \cdot 10^4$$

$$I_E := \frac{V_{BB} - V_{BE} - V_m}{\frac{R_{BB}}{1 + \beta} + R_E} \quad I_E = 2.557 \cdot 10^{-3}$$

$$r_e := \frac{V_T}{I_E} \quad r_e = 9.777$$

## AC Solutions

This first solution uses the equations involving  $R_{tc}$ , even though  $R_{tc} = 0$ . It is based on the Thevenin emitter circuit which have  $v_{eoc}$  in series with  $r_{ieo}$ .

$$v_{tb} := v_s \cdot \frac{R_P(R_1, R_2)}{R_S + R_P(R_1, R_2)} \quad v_{tb} = 0.916$$

$$R_{tb} := R_P(R_S, R_P(R_1, R_2)) \quad R_{tb} = 4.58 \cdot 10^3$$

$$R_{te} := R_P(R_E, R_L) \quad R_{te} = 3.59 \cdot 10^3$$

$$r_{ie} := \frac{R_{tb} + r_x}{1 + \beta} + r_e \quad r_{ie} = 55.779$$

$$R_{tc} := R_C \quad R_{tc} = 0$$

$$v_{eoc} := v_{tb} \cdot \frac{r_0 + \frac{R_{tc}}{1 + \beta}}{r_{ie} + r_0 + \frac{R_{tc}}{1 + \beta}} \quad v_{eoc} = 0.915$$

$$r_{ieo} := r_{ie} \cdot \frac{r_0 + R_{tc}}{r_{ie} + r_0 + \frac{R_{tc}}{1 + \beta}} \quad r_{ieo} = 55.717$$

$$v_o := v_{eoc} \cdot \frac{R_P(R_E, R_L)}{r_{ieo} + R_P(R_E, R_L)} \quad v_o = 0.901 \quad \text{This is the voltage gain.}$$

$$r_{out} := R_P(R_E, r_{ieo}) \quad r_{out} = 55.168$$

$$r_{out} := R_p(r_{ieo}, R_E) \quad r_{out} = 55.168$$

$$r_{ib} := r_x + (1 + \beta) \cdot (r_e + R_p(R_{te}, R_{tc} + r_0)) - \frac{\beta \cdot R_{tc} \cdot R_{te}}{R_{tc} + r_0 + R_{te}}$$

$$r_{ib} = 3.359 \cdot 10^5$$

$$r_{in} := R_p(r_{ib}, R_p(R_1, R_2)) \quad r_{in} = 4.693 \cdot 10^4$$

The following solution is based on the emitter equivalent circuit. It is the preferred solution when  $R_{tc} = 0$ . Note that this is an exact solution, where  $r_0$  is considered to be an external resistor. The answers are the same as the ones in the solution above.

$$v_o := v_{tb} \cdot \frac{R_p(R_E, R_p(r_0, R_L))}{r_{ie} + R_p(R_E, R_p(r_0, R_L))} \quad v_o = 0.901 \quad \text{This is the voltage gain.}$$

$$r_{out} := R_p(r_{ie}, R_p(r_0, R_E)) \quad r_{out} = 55.168$$

$$r_{ib} := r_x + (1 + \beta) \cdot (r_e + R_p(R_E, R_p(r_0, R_L))) \quad r_{ib} = 3.359 \cdot 10^5$$

$$r_{in} := R_p(r_{ib}, R_p(R_1, R_2)) \quad r_{in} = 4.693 \cdot 10^4$$

Note the low output resistance of the CC amplifier. It is much lower than the output resistance in the CE amplifier example. To obtain a high voltage gain and a low output resistance, a CE/CC amp can be used in cascade. We will look at such an example.